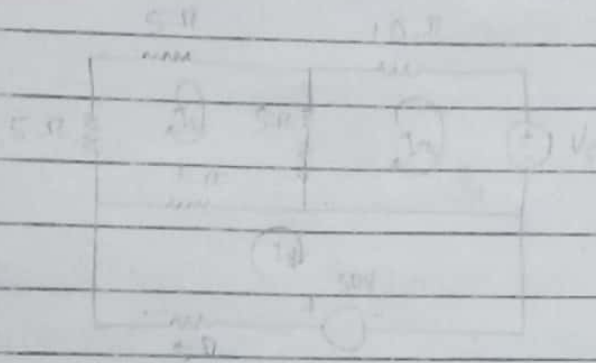


Assignment (EDC)

Solving circuits using mesh and nodal analysis

- 1 Find V_s in figure 1, so that current in $10\text{-}\Omega$ resistor would be i) 5A ii) 0A .



Soln

Using mesh analysis

In mesh 1,

$$50 - 5I_1 - 5(I_1 - I_2) = 0$$

$$\text{or, } 50 - 10I_1 + 5I_2 = 0$$

$$\text{or, } 5 - 2I_1 + I_2 = 0 \quad \text{--- (i)}$$

In mesh 2,

$$5(I_2 - I_1) + 10I_2 + 5(I_2 - I_3) = 0$$

$$\text{or, } 20I_2 - 5I_1 - 5I_3 = 0$$

$$\text{or, } 4I_2 - I_1 - I_3 = 0 \quad \text{--- (ii)}$$

In mesh 3,

$$V_s - (-10I_3) + 5(I_3 - I_2) = 0$$

$$\text{or, } V_s + 15I_3 - 5I_2 = 0 \quad \text{--- (iii)}$$

When current is 5A in $10\text{-}\Omega$ resistorSolving (i) and (ii) and putting $I_3 = 5\text{A}$, and solving (iii)

$$I_1 = -3.57\text{A} \quad I_2 = -2.14\text{A}$$

$$\therefore V_s = 64.3\text{V}$$


When current in 10Ω resistor is $0A$.

$$I_1 = \frac{-20}{7} A = -2.85A$$

$$V_S = 3.57V$$

$$I_2 = \frac{-5}{7} A = -0.714A$$

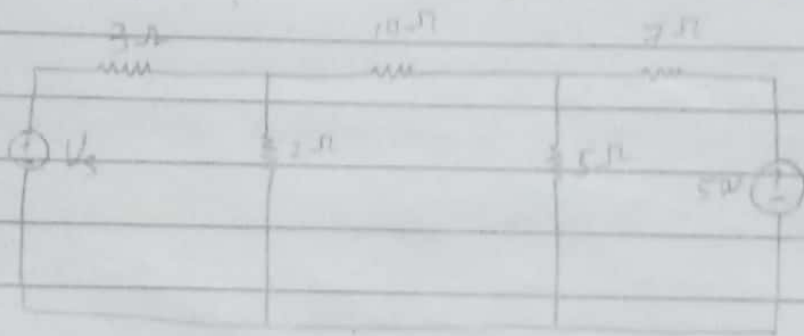2. Find V_S in figure 2, so that current in 10Ω is zero amperes using
 i) Mesh analysis ii) Nodal analysis.



Solⁿ: i) Using mesh analysis

In mesh 1,

$$V_S - 3I_1 - 2(I_1 - I_2) = 0$$

$$\text{or, } V_S - 5I_1 + 2I_2 = 0 \quad \text{--- (i)}$$


In mesh 2,

$$-2(I_2 - I_1) - 10I_2 - 5(I_2 - I_3) = 0$$

$$\text{or, } 17I_2 - 2I_1 - 5I_3 = 0 \quad [I_2 = 0A]$$

$$\text{or, } 17I_2^0 - 2I_1 = 5I_3 \quad \therefore 2I_1 = -5I_3 \quad \text{--- (ii)}$$

In mesh 3,

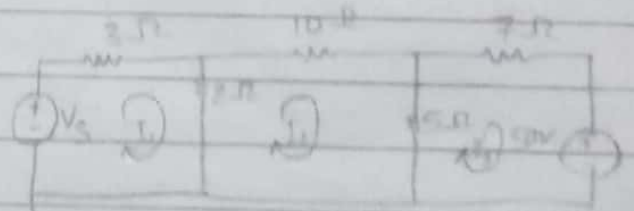

$$-5(I_3 - I_2) - 7I_3 - 50 = 0 \quad [\because I_2 = 0]$$

$$12 I_3 + 5 I_2 + 50 = 0$$

$$I_3 = \frac{50}{12} \text{ A} = 4.16 \text{ A}$$


$$I_1 = -10.41 \text{ A}$$

Now, in eqn (i)

$$V_s - 5(-10.41) + 2 \times 0 = 0$$

$$V_s = 52.05 \text{ V}$$

Using nodal analysis

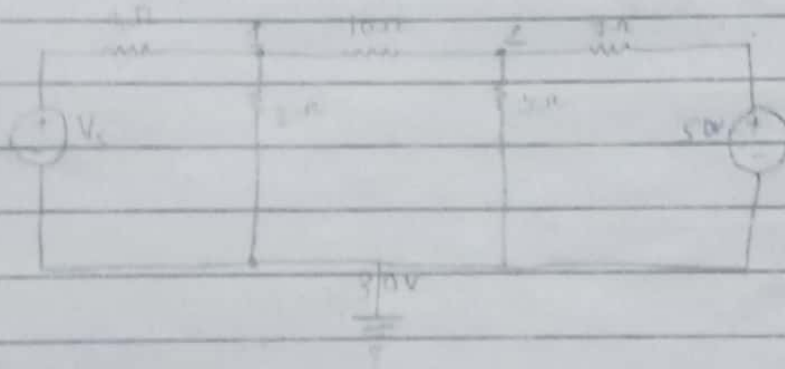

At node 1,

$$\frac{V_1 - V_s}{3} + \frac{V_1 - V_2}{10} + \frac{V_2 - V_s}{2} = 0$$

$$\frac{V_1}{3} + \frac{V_2}{2} - \frac{V_s}{3} = 0$$

At node 2,

$$\frac{V_2 - V_3 - 50}{7} + \frac{V_2 - V_3}{5} + \frac{V_2 - V_1}{10} = 0$$


$$\frac{V_2 + V_2}{7} = \frac{50}{7}$$

$$\text{or, } \frac{12}{35} V_2 = \frac{50}{7}$$

$$\text{or, } V_2 = 20.83V \quad V_1 = 20.83V$$

Putting V_1 and V_2 in eqn ① we get,
 $V_3 = 50.08V$

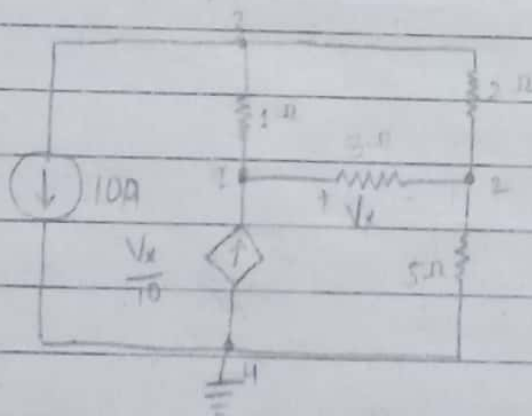3. In the network shown in figure 3, find the current in each resistor using Nodal analysis



$$\text{At node 1, } \frac{V_x}{10} + \frac{V_1 - V_3}{1} + 10 = 0$$

$$\text{or, } \frac{V_x}{10} + V_1 - V_3 + 10 = 0$$

$$\text{At node 2, } \frac{V_2 - V_3}{2} + \frac{V_2}{5} + \frac{V_2 - V_1}{3} = 0$$

$$\text{or, } \frac{V_1 - V_x - V_3}{2} + \frac{V_2 - V_x}{5} - \frac{V_x}{3} = 0$$

$$\text{or, } \frac{V_1 - V_x - V_3}{2} + \frac{V_1 - V_x}{5} - \frac{V_x}{3} = 0$$

$$\text{or, } \frac{7}{10} V_1 - \frac{31}{30} V_x - \frac{V_3}{2} = 0 \quad \text{--- (II)}$$

Solving (I) (II) and (III)

$$V_1 = 183.33 \text{ V}, V_3 = 177.19 \text{ V}, V_x = 38.46 \text{ V},$$

$$V_2 = V_1 - V_x$$

$$= 183.33 - 38.46$$

$$= 144.87 \text{ V}$$

In 1Ω resistor,

$$I_1 = 6.14 \text{ A}$$

In 2Ω resistor,

$$I_2 = \frac{144.87 - 177.19}{2}$$


$$= 16.16 \text{ A}$$

In 3Ω resistor,

$$I_3 = \frac{38.46}{3} = 12.82 \text{ A}$$

$$\text{In } 5 \Omega \text{ resistor, } I_5 = \frac{144.87}{5} = 28.94 \text{ A}$$

4.

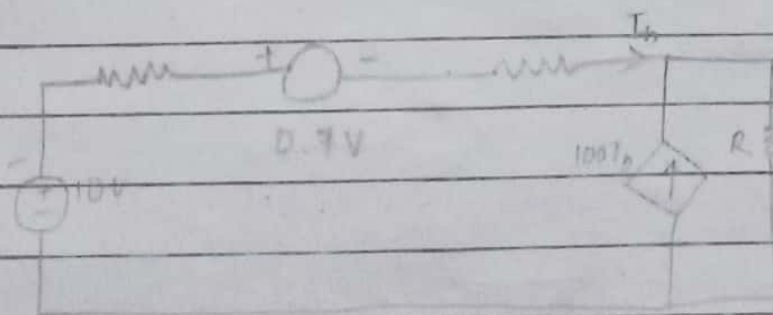


Use mesh analysis to find voltage across (R) in figure 4, when i) $R=100\ \Omega$ ii) $R=2\ \Omega$

Solⁿ

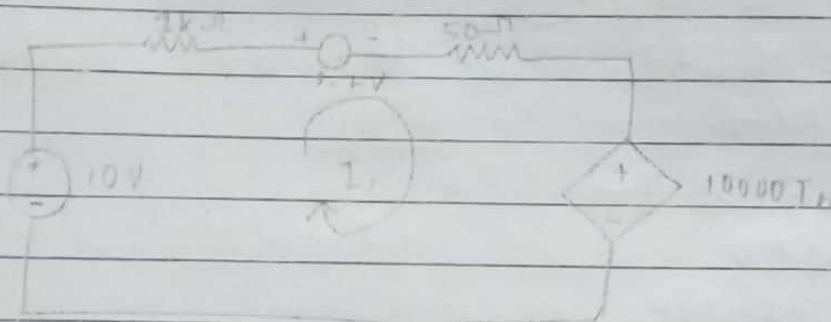i) When $R=100\ \Omega$,

converting current source into voltage source,




Using mesh analysis,

$$10 - 1000I_b - 0.7 - 50I_b - 10000I_b = 0$$

$$\text{or, } I_b = 8.34 \times 10^{-4} \text{ A}$$

$$\begin{aligned} V_R &= 100I_b \times R \\ &= 8.34 \times 10^{-4} \times 100 \\ &= 0.083 \text{ V} \end{aligned}$$

ii) When $R=2\ \Omega$, the ckt becomes

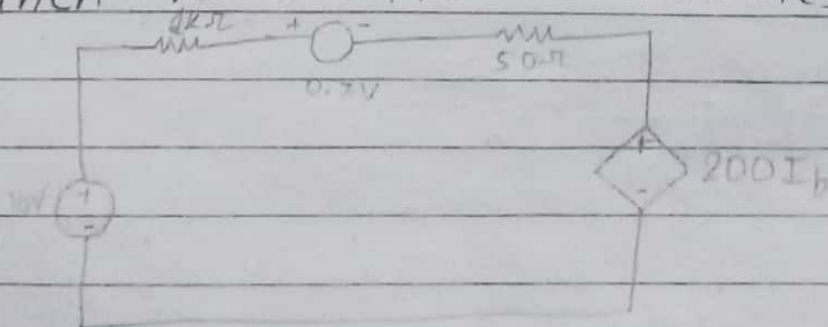

Now,

$$10 - 1000 I_b - 0.7 - 50 I_b - 200 I_b = 0$$


$$I_b = 7.44 \times 10^{-3} \text{ A}$$

$$V = 200 I_b \times R$$


$$= 200 \times 7.44 \times 10^{-3} \times 2$$

$$= 2.976 \text{ V}$$

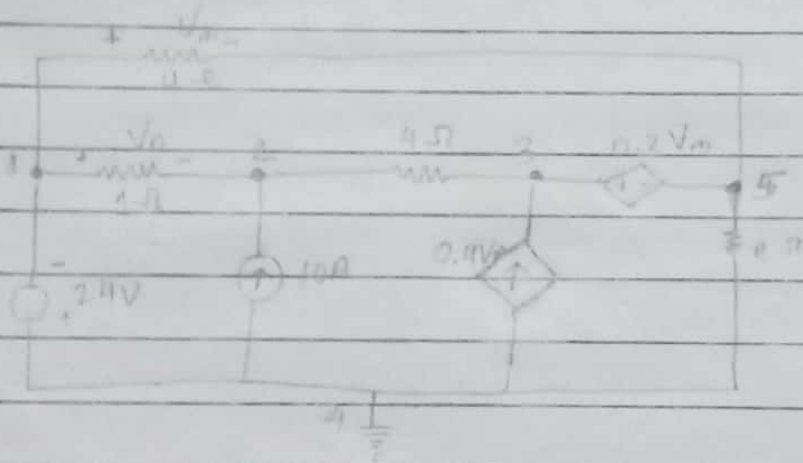5. Determine the current through each resistor of the circuit shown in figure 5 using Nodal analysis.



Solⁿ

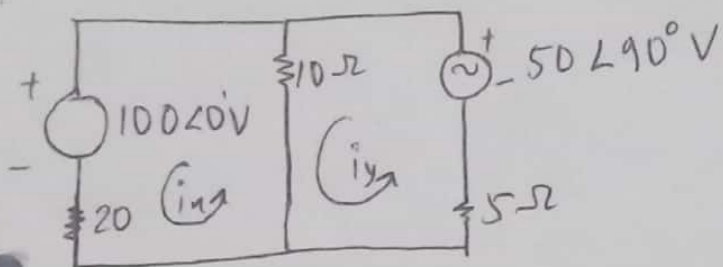

In mesh 1,

$$-100 - 20i_x - 10(i_x - i_y) = 0$$

$$\text{or, } 10 + 3i_x - i_y = 0 \quad \text{--- (I)}$$

In mesh 2,

$$50j - 10(i_y - i_x) - 5i_y = 0$$

$$\text{or, } 50j - 15i_y + 10i_x = 0 \quad \text{--- (II)}$$

~~the~~ Using Cramer's rule,

component of i_x

i_y	constant
3	10
10	$50j$

$$D_x = \begin{vmatrix} 10 & -1 \\ 50j & -15 \end{vmatrix} = -150 + 50j$$

$$D_y = \begin{vmatrix} 3 & 10 \\ 10 & 50j \end{vmatrix} = 150j - 100$$

$$D = \begin{vmatrix} 3 & -1 \\ 10 & -15 \end{vmatrix} = -35$$

$$i_x = \frac{D_x}{D} = \frac{-150 + 50j}{-35} = \frac{30}{7} - \frac{10}{7}j$$

$$i_y = \frac{D_y}{D} = \frac{150j - 100}{-35} = \frac{20}{7} - \frac{30}{7}j$$

9. i) mesh analysis.
in mesh 1,

$$5(i_1 - i_3) - 10j + 10(i_1 - i_2) = 0$$

$$\text{or, } 15i_1 - 10i_2 - 5i_3 - 10j = 0 \quad \text{--- (I)}$$

in mesh 2,

$$5j - 10 \angle 30^\circ + 8(i_2 - i_3) + 10(i_2 - i_1) = 0$$

$$\text{or, } 5j - 5\sqrt{3} - 5j + 18i_2 + 10i_1 - 8i_3 = 0$$

$$\text{or, } 10i_1 + 18i_2 - 8i_3 - 5\sqrt{3} = 0 \quad \text{--- (II)}$$

in mesh 3,

$$4j \cdot i_3 + 3i_3 - 20 + 5(i_3 - i_1) + 8(i_3 - i_2) = 0$$

$$\text{or, } 4j \cdot i_3 + 3i_3 - 20 + 15i_3 - 5i_1 - 8i_2 = 0$$

$$\text{or, } 4j \cdot i_3 + 16i_3 - 5i_1 - 8i_2 - 20 = 0$$

$$\text{or, } 5i_1 + 8i_2 + (16 + 4j)i_3 - 20 = 0 \quad \text{--- (III)}$$

Using Cramer's Rule,

	i_1	i_2	i_3	constant
15	-10	-5	-10j	$D = \begin{vmatrix} 15 & -10 & -5 \\ 10 & 18 & -8 \\ 5 & 8 & 16+4j \end{vmatrix}$ $= 7330 + 1480j$
10	18	-8	-5\sqrt{3}	
5	8	16+4j	-20	

$$D_x = \begin{vmatrix} -10j & -10 & -5 \\ -5\sqrt{3} & 18 & -8 \\ -20 & 8 & 16+4j \end{vmatrix} = -519.23 - 3866.41j$$

$$D_y = \begin{vmatrix} 15 & -10j & -5 \\ 10 & -5\sqrt{3} & -8 \\ 5 & -20 & 16+4j \end{vmatrix} = -4094.97 + 1480.39j$$

$$D_z = \begin{vmatrix} 15 & -10 & -10j \\ 10 & 18 & -5\sqrt{3} \\ 5 & 8 & -20 \end{vmatrix} = -5927.74 + 100j$$

$$i_1 = \frac{-519.23 - 3866.41j}{-5927.74 + 100j} = -0.17 - 0.493j$$

$$i_2 = \frac{-4094.97 + 1480.39j}{-5927.74 + 100j} = -0.23 - 1.09j$$

$$i_3 = \frac{-5927.74 + 100j}{-5927.74 + 100j} = -0.77 + 0.19j$$